Computer organization, Spring 2018

Lab 6: Pipeline CPU II

Due: 2018/06/23 (SAT) 23:59:59

1. Goal

In Lab6, you need to modify the CPU designed in Lab5 and implement an advanced version pipelined CPU which can handle hazard.

2. Demands

- A. Please use ModelSim or Xilinx as your HDL simulator.
- B. One person forms a group. Please attach your name and student ID as comments in the top of the file. (Ex. Lab6_Student ID.zip) The type of compressed file must be "zip". (Other form of file will get -10%.)
 The assignment you upload on E3 must have the form of "Lab6_student ID.zip".
- C. Testbench .v is supplied.

3. Data/Control Hazard description

a. Code:

Data hazard:

ADD, ADDI, SUB, AND, OR, NOR, LUI, SLT, SLL, LW and SW.

- Need to implement Hazard Detection and Forwarding

(i.e. Forwarding.v and HazardDetectionUnit.v)

- Need to **stall** pipelined CPU if it detects **load-use**.
- Need to **forward** data if instructions have data dependency.

(Bonus) Control hazard:

BEQ, BNE, JUMP

Modify Hazard Detection Unit. Once a branch instruction is taken or a jump instructions performed, you should flush the IF/ID, ID/EX, and EX/ MEM pipeline registers, and then fetch the correct instruction from the new PC value

b. Testbench:

Please use CO_P6_test_1.txt to test data hazard, CO_P6_test_2.txt to test control hazard.

```
CO_P6_test_1.txt
```

```
addi $1, $0, 5
```

addi \$2, \$0, 2

addi \$3, \$0, 11

addi \$4, \$0, 6

sw \$1, 4(\$0)

addi \$7, \$1, 10

lw \$5, 4(\$0)

and \$8, \$5, \$3

Result:

r1=5; r2=2; r3=11; r4=6; r5=5; r7=15; r8=1; r29=128;

data_mem[1]=5;

others are 0.

CO_P6_test_2.txt

addi \$1, \$0, 2

addi \$2, \$0, 2

addi \$3, \$0, 2

addi \$4, \$0, 4

addi \$5, \$0, -1

beq \$1, \$2, L1

slt \$9 \$2, \$4

sw \$1, 4(\$0)

or \$10 \$1, \$4

L1: addi \$6, \$0, 2

addi \$1, \$1, 3

addi \$2, \$2, 3

and \$7, \$3, \$4

sub \$8, \$5, \$3

Result:

r1=5; r2=5; r3=2; r4=4; r5=-1; r6=2; r7=0; r8=-3; r29=128;

data_mem[1]=0


others are 0.

c. Report:

The context must include and the report is at most 3 pages.

- : 1. HDL simulator you used
 - 2. Finished part
 - 3. Architecture diagrams
 - 4. Hardware module analysis
 - 5. Problems you met and solutions
 - 6. Summary

4. Architecture

 

5. Grade

Total score: 100+20 bonus pts. COPY WILL GET A 0 POINT!

a. Data hazard: 80 pts

b. (bonus) Control hazard: 20 pts

c. Report: 20 pts

d. incorrect file form: -10pts

6. Hand in your assignment

Please upload the assignment to the E3.

Put all of *.v source files and report into same compressed file.

(Use your student ID to be the name of your compressed file and must have the form of "Lab6_student ID.zip")

7. Q&A

If you have any question, just send email to TA (coco335715@gmail.com).